

# How to Fry an IGCT in 1 $\mu\text{s}$ or Less


Kirk T. McDonald

Joseph Henry Laboratories, Princeton University, Princeton, NJ 08544

(April 17, 2004)
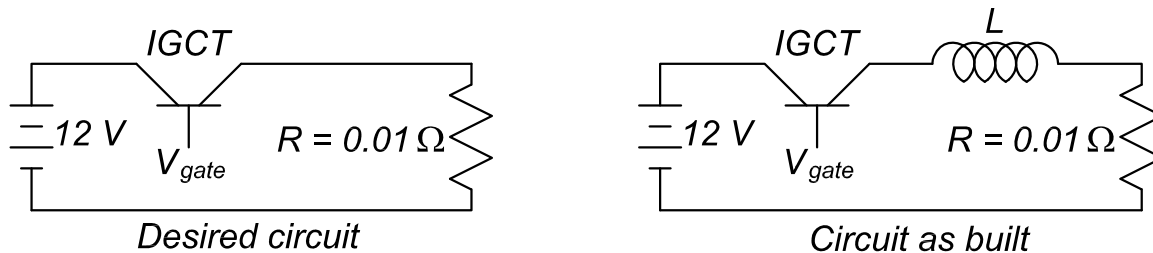
## 1 Problem

An IGCT (= Integrated Gate Commutated Thyristor<sup>1</sup>) is a kind of transistor that can switch thousands of amps of current in 1  $\mu\text{sec}$ . It was desired to test an IGCT with 1200 amps of current from a 12 V automobile battery. The proposed test circuit is shown on the left in the figure below, in which a load resistor of  $0.01 \Omega$  was attached to the output of the IGCT. For this a 10 m length of welding cable was used, whose insulation had a diameter of 1 cm.



The technician neatly coiled the welding cable into a bundle consisting of 10 circular turns in a stack 10 cm high. It was not noticed that this coil forms an inductor. Thus, the circuit as actually built is sketched on the right of the above figure.

1. Estimate the self inductance  $L$  of the coil of welding cable supposing that the coil were a “long” solenoid.
2. How long would it take for the current to reach 600 amps once the IGCT switch is turned on, supposing that the switch acted instantaneously.
3. How much energy is stored in the inductor once the current has reached its maximum value?
4. How much energy would be required to ionize every atom in the junction of the IGCT, supposing that the junction has an area of  $4 \text{ cm}^2$ , a thickness of  $1 \mu\text{m}$ , and that each atom occupies a volume of  $(2 \text{ angstrom})^3$  and has an ionization potential of 10 volts.
5. Some time after the current has risen to the full 1200 A, the IGCT is switched off (by applying an appropriate voltage  $V_{gate}$  to the base). What is the voltage across the inductor during the 1  $\mu\text{sec}$  that the IGCT is switching the current off?
6. The IGCT has a maximum voltage rating of 5 kV (and a cost of  $\approx \$3000$ ). Did it survive this test?

---

<sup>1</sup><http://www.abb.com/semiconductors>

## 2 Solution

1. The self inductance  $L$  of a coil can be calculated from the magnetic flux  $\Phi$  through the coil when it carries current  $I$ , according to

$$\Phi = LI. \quad (1)$$

Regarding the 10-turn coil as a “long” solenoid of radius  $r = 10 \text{ m} / 10 / 2\pi = 1/2\pi$  and length  $l = 0.1 \text{ m}$ , the magnetic field  $B$  due to current  $I$  is parallel to the axis, essentially uniform inside the coil, and nearly zero outside it. Then, using Ampere’s law for a rectangular loop with one edge parallel to the axis and closer to it than the radius  $r$  we have

$$Bl = \mu_0 NI, \quad \text{and} \quad B = \frac{\mu_0 NI}{l}. \quad (2)$$

where  $N = 10$  is the number of turns. The magnetic flux through the coil associated with this field is

$$\Phi = NB\pi r^2 = \frac{\mu_0 N^2 \pi r^2 I}{l}, \quad (3)$$

and hence the self inductance is

$$L = \frac{\mu_0 N^2 \pi r^2}{l} = \frac{4\pi \times 10^{-7} \cdot 10^2 \cdot \pi}{(2\pi)^2 \cdot 0.1} = 10^{-4} \text{ H}. \quad (4)$$

2. After the switch is closed, the current in the circuit rises exponentially with time constant  $\tau = L/R = 10^{-4}/0.01 = 0.01 \text{ s}$ . In detail, the circuit equation is

$$V_{\text{battery}} = L \frac{dI}{dt} + IR, \quad (5)$$

whose solution is

$$I = \frac{V_{\text{battery}}}{R} (1 - e^{-Rt/L}), \quad (6)$$

supposing that the switch was closed at time  $t = 0$ . The current reaches one half maximum at time  $t$  such that  $e^{-Rt/L} = 1/2$ , *i.e.*, when

$$t = \frac{L}{R} \ln 2 = 0.007 \text{ s}. \quad (7)$$

3. The energy stored in the inductor is

$$U = \frac{1}{2} LI^2 = 0.5 \cdot 10^{-4} (1200)^2 = 72 \text{ Joules}. \quad (8)$$

4. The IGCT junction has a volume of  $1 \mu\text{m} \cdot 4 \text{ cm}^2 = 10^{-6} \cdot 4 \cdot (10^{-2})^2 = 4 \times 10^{-10} \text{ m}^3$ . A silicon atom has a volume of  $(2 \text{ angstrom})^3 = (2 \times 10^{-10})^3 = 8 \times 10^{-30} \text{ m}^3$ . The number of atoms in the junction is  $4 \times 10^{-10} / 8 \times 10^{-30} = 5 \times 10^{19}$ . If the ionization potential of silicon is 10 volts, it takes  $10 \text{ eV} = 1.6 \times 10^{-18} \text{ Joules}$  of energy to ionize an atom, and hence  $5 \times 10^{19} \cdot 1.6 \times 10^{-18} = 80 \text{ Joules}$  to ionize every atom in the junction.

Thus, the energy stored in the inductor, if applied to ionizing atoms in the junction of the IGCT, would be sufficient to completely ionize the junction. However, even if the junction is only partially ionized it would fail.

5. When the IGCT is switched off it forces the current to zero in 1  $\mu\text{sec}$ , so in the present example the rate of change of the current would be  $dI/ = 1200 \text{ A}/10^{-6} \text{ s} = 1.2 \times 10^9 \text{ A/s}$ . The resulting voltage drop across the inductor formed by the welding cable was

$$\Delta V = L \frac{dI}{dt} = 10^{-4} \text{ H} \cdot 1.2 \times 10^9 \text{ A/s} = 120,000 \text{ V}. \quad (9)$$

Note also that  $\Delta V = V_{\text{battery}} \cdot \tau / 10^{-6} = 10,000 V_{\text{battery}}$ . The IGCT forces the current to change 10,000 times faster than the “natural” time scale of  $\tau = L/R$ , and consequently a voltage 10,000 times that of the battery is developed across the inductance in the circuit.

6. The 120,000 volts across the inductor also appeared across the IGCT, which is rated for only 5,000 volts. In practice, the IGCT survived for about  $1/3 \mu\text{s}$ , dropping the current from 1200 to 800 amps. It then failed by forming an internal “short” and the current jumped back up to 1200 amps (since very little of the energy stored in the inductor had been dissipated in shorting the IGCT).